




Problem #4

GOALS

- Create circuit diagrams from Boolean expression and vice versa
- Create Boolean expression and circuit diagram from truth table
- Simplify Boolean expression
- Experiment with adders and other logic circuits

Exercise 1:

1. For the following circuit diagram,

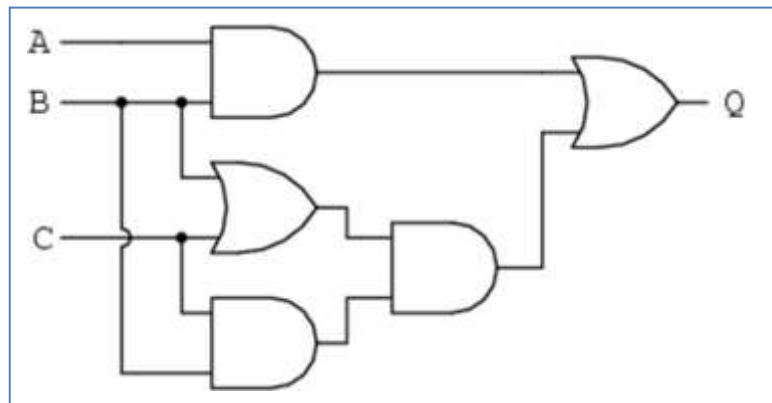

- Apply the rules of Boolean algebra to reduce the expression to its simplest form (simplest defined as requiring the fewest gates to implement).
- Implement the simplified expression with the “Logic Gates” applet and take a screenshot.

Exercise 2:


1. Start the “Logic Gates” applet.
2. Add two switches, one XOR and one output, and connect them.
3. Press the *Run* button and try out all four combinations of inputs for the switches, recording the results in a truth table (you should create a separate truth table in your word document and not a truth table in your applet!). Take 4 screenshots for each of those four possible combinations.

Exercise 3:

1. Start the “Logic Gates” applet again.
2. Create the same circuit as previously, but this time insert a NOT box between XOR and the output.
3. Press the *Run* button and try out all 4 values by changing the switch values. You do not have to take screenshots, but again record the results in a truth table (create a separate truth table in your word document and not a truth table in your applet!) so you can see the values.

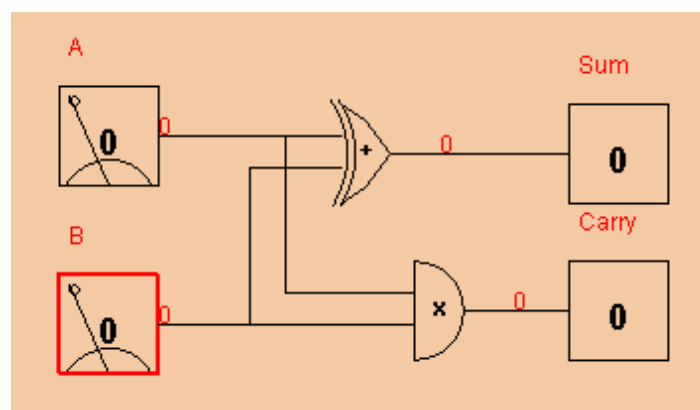Exercise 4:

Create the following half adder using the “Logic Gates” applet.





- Write the truth table for this circuit. There are two inputs and two outputs.
- Test the circuit using the applet. Make sure you label your switches (inputs) and outputs. Take a screenshot of the circuit that is created by the “Logic Gates” applet.

Exercise 5:


- Given the following truth-table, where W is the output.

A	B	C	W
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Implement the simplified expression with “Logic Gates” applet, and insert a screenshot here.

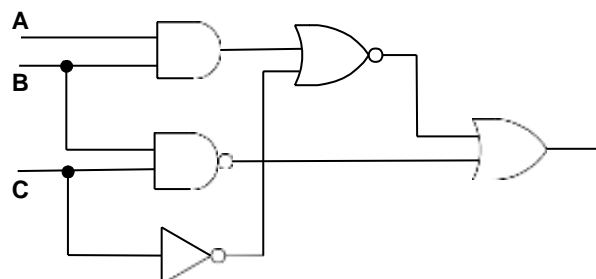Exercise 6:

- Use the “Logic Gates” applet to implement the following circuit and take a screenshot.



- Analyze the behavior of the above circuit with a truth table and show the table here?